

Course: EE787 – Memory Design and Testing
Department of Electrical Engineering
Indian Institute of Technology, Delhi

Major Test, Winter Semester, Session 2010-2011
Date: 7th May, 2011

Max Marks: 40

All 4 questions are to be answered Time allowed: 90 mins.

- 1) Following questions are to be answered in brief, preferably in point form. Verbose answers will possibly attract penalty.
- a. Why are sense amplifiers located between memory array and column decoder but not between row decoder and memory array? (2)
 - b. What are the main differences between the following two possibilities of embedded DRAM on a logic chip:
 - i. Case 1: Use a trench capable process (2)
 - ii. Case 2: Use a regular process with poly-caps as storage capacitors.
 - c. Imagine the part of a cache controller that is responsible for transferring data from the main DRAM to a local SRAM cache line. The cache line width is a multiple of the memory bus width. Which property of SDRAMs (SDR or DDR) helps in this situation and why? (2)
 - d. What is the maximum memory access bandwidth of a 64bit wide, 200MHz DDR SDRAM with the following access latencies: (3-2-2.5-0.5) (block select – row decode – column decode – burst cycle)? What is the typical memory access bandwidth when a new random address is periodically applied after 4 words read? (2)
 - e. Which RAM-type do you select for:
 - i. a network processor with 4GByte of memory (2)
 - ii. a single-chip search engine with a table size of 1024x1024 bit, access freq. of 300MHz required? (2)
- 2) Consider a DRAM with 2Mb storage and data I/O DQ x2. The array is configured as 8 blocks of 256Kb each. (1024 rows, 512 columns, folded bitline)
- a. How many I/O lines are needed the array? (1)
 - b. How big is a page of data? (Recall the definition of a page from NAND flash context) (1)
 - c. Sketch a decoding scheme. Show only the block schematic with bus widths etc. (2)
 - d. Assume 3 bits is globally decoded and others are locally decoded. How many these bit needed to be routed to each array? (1)
 - e. Draw the floorplan of the array and show the routing of the address, data and key control signals. (3)
 - f. Draw the gate level schematic of the block address decoder. (2)
- 3) Consider the folded-area DRAM core architecture in figure 1.
- a. What problems do you foresee in the sensing scheme? Would the problem be mitigated if we put many sense enable transistors instead of one? (3)
 - b. Provide the gate level design of the column decoder (4)
 - c. Outline any problems you see in the signal levels on the I/O and I/O complement lines. Provide a solution to the problem (3)